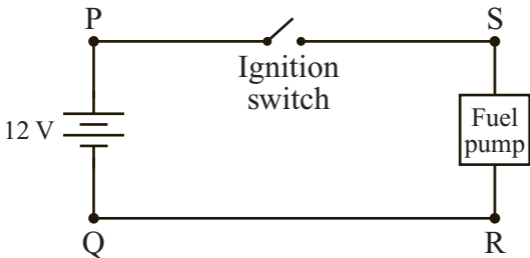


34

The diagram below represents a circuit to a fuel pump in a car. The ignition switch is turned off.



This fuel pump may have an internal short circuit. At which two points should an ohmmeter be connected to measure the resistance of the fuel pump?

- A. P and S
- B. Q and P
- C. R and Q
- D. S and R